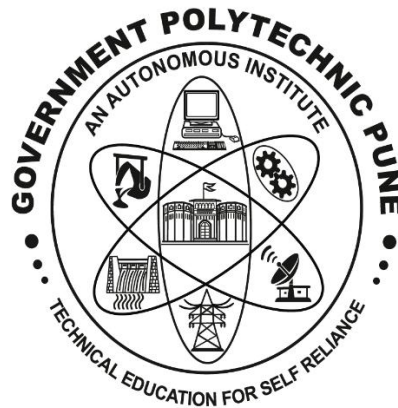


GOVERNMENT POLYTECHNIC COLLEGE

PUNE DIST.PUNE

2024 -2025

DEPARTMENT OF COMPUTER ENGINEERING



A MICROPROJECT REPORT ON “Full Wave (Bridge) Rectifier With C Filter”

**For the partial fulfillment of Diploma in Computer Engineering,GP
Pune.**

Guided by

Pranali G Gahukar mam

Submitted by

Sr. No	Name of the student	Enrollment No.
1	Tekade Satyajit Ashok	2406204
2	Shinde Pranay Prabhakar	2406185
3	Vardekar Prathamesh Dinesh	2406209
4	Sonawane Sumedh Sahebrao	2406191


- **Title:**

Full wave Rectifier (Bridge) with C filter

- **Resources Required:**

1. Transformer : (230V to 12V)
2. Diodes : Four
3. Resistor : 1 kohm
4. Connecting Wires
5. PCB
6. Multimeter (for testing output voltage)

- **Circuit Diagram:**

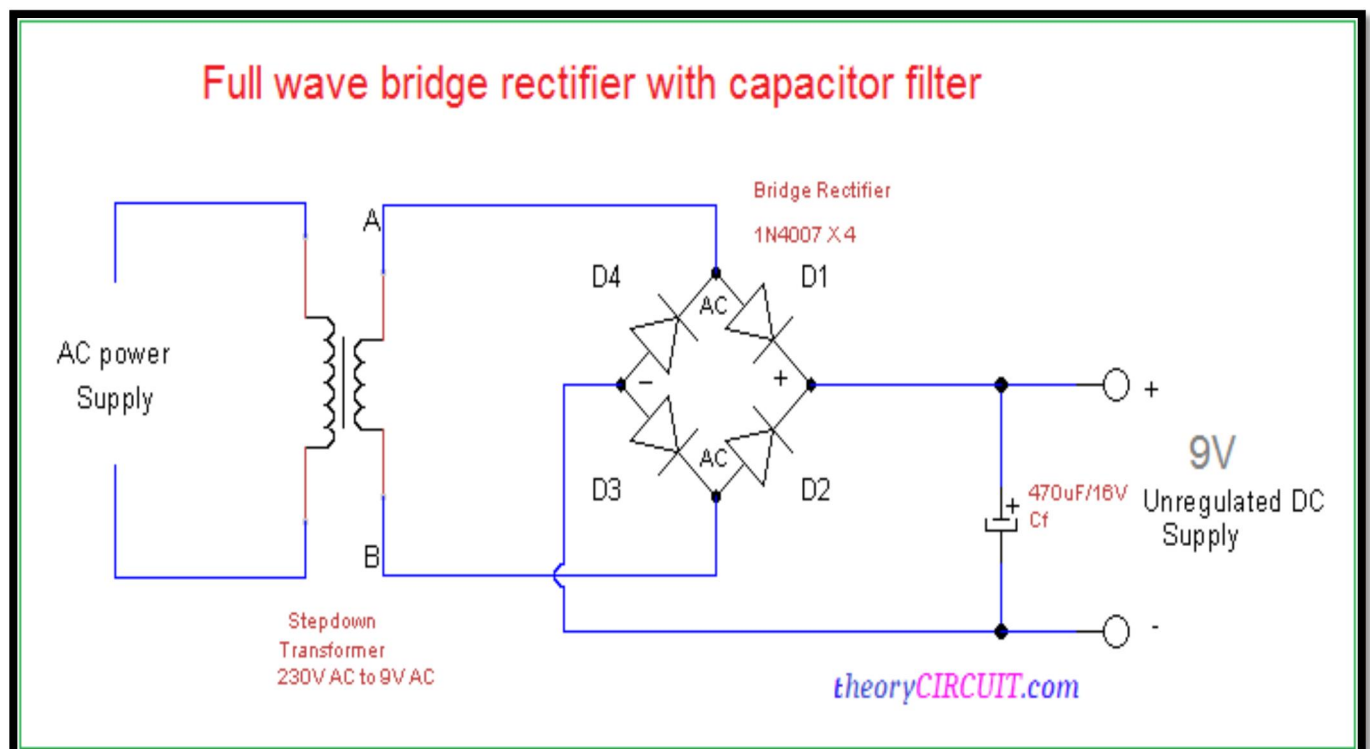

Procedure:

1. Assemble the Circuit:

- Connect four diodes in a bridge configuration (D1, D2, D3, and D4) as shown in the diagram.
- Connect the output of the bridge rectifier to a load resistor (100Ω) in series with the capacitor ($1000\mu\text{F}$) placed parallel to the load resistor.
- Connect the AC input to the bridge rectifier, and ensure the correct polarity for the diodes.
- Use an oscilloscope to monitor the waveform at the output of the bridge rectifier.

2. Initial Test:

- Power on the AC supply to the circuit. Observe the rectified waveform using the oscilloscope.
- Without the capacitor, the waveform should appear as a pulsating DC (rectified signal) that fluctuates between 0V and the peak value of the AC input.

3. Add the Capacitor Filter:

- Insert the capacitor in parallel with the load resistor. This will filter out some of the ripple.
- Observe the waveform again with the oscilloscope. The waveform should now appear smoother with reduced ripple, approximating a constant DC voltage.

4. Measure the Output Voltage:

- Measure the DC output voltage across the load resistor using the multimeter.
- Record the peak DC voltage and compare it with the expected output (approximately equal to the peak of the AC input voltage).

5. Observe the Ripple:

- Measure the ripple voltage by observing the fluctuations in the output waveform on the oscilloscope. The ripple should be smaller after adding the capacitor filter.

Working:

1. Full-Wave Bridge Rectifier:

- The AC input signal alternates between positive and negative half cycles.
- During the **positive half cycle**, diodes **D1** and **D4** conduct, allowing current to flow through the load resistor in one direction.
- During the **negative half cycle**, diodes **D2** and **D3** conduct, ensuring that the current still flows through the load resistor in the same direction.
- This results in a pulsating DC output, where the current flows in only one direction but the voltage fluctuates between 0V and the peak AC voltage.

2. Capacitor Filter:

- The capacitor **C** charges up to the peak value of the rectified output during each half cycle when the rectified voltage is above the capacitor's voltage.
- When the rectified voltage drops below the capacitor's voltage, the capacitor discharges slightly, helping to maintain the output voltage and filling in the gaps.
- This reduces the ripple in the output and provides a smoother DC voltage.

3. Smoothing the Output:

- The capacitor reduces the fluctuations in the DC output voltage by providing charge during the "off" periods of the rectified waveform. This makes the output closer to a constant DC voltage, with a small ripple depending on the load and the size of the capacitor.

Observations:

- **Without the Capacitor:** The output voltage is pulsating DC. The voltage fluctuates between 0V and the peak value of the AC input, which means there is a high ripple.
- **With the Capacitor:** The output voltage is smoother. The capacitor charges to the peak voltage and helps to reduce the ripple, giving a more stable DC output.
- **Measured Output Voltage:** The DC output voltage should be approximately equal to the peak of the AC input. For an AC input of 120V RMS, the peak voltage would be $V_{\text{peak}} = 120\text{V} \times \sqrt{2} \approx 170\text{V}$.
- **Ripple Voltage:** The ripple voltage depends on the size of the capacitor and the load resistance. With a 1000 μF capacitor, the ripple should be significantly reduced, but there might still be minor fluctuations.

Results:

- **Input AC Voltage (RMS):** 120V
- **Peak AC Voltage:** 170V
- **Output DC Voltage (with filter):** Approximately 170V (with small ripple)
- **Ripple Voltage:** Measured using the oscilloscope, typically a few volts depending on the load and capacitor.

Conclusion:

- The **Full-Wave Bridge Rectifier** effectively converts AC into DC, utilizing both positive and negative half-cycles of the AC input.
- The **Capacitor Filter** significantly smooths the pulsating DC output by reducing the ripple, but it does not eliminate it completely.
- The output DC voltage is approximately equal to the peak AC voltage, with minor fluctuations depending on the filter capacitance and load.